



FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรตีอัมและตัดสายโทรศัพท์ (ไม่ใช้ไฟ)
TELEPHONE CUT OFF TIMER 1-20 MIN.
CODE 322

จึงจะต้องห้ามกู้สายให้ใหม่

ข้อมูลทางด้านเทคนิค

- ไม่ใช้ไฟ
- สามารถตั้งเวลาตัดสายโทรศัพท์ได้ตั้งแต่ 1- 20 วินาที
- มีสี - กรณีต้องการตัดสายโทรศัพท์
- ตัดสายโทรศัพท์ เมื่อมีการตีอัมยาวประมาณ 20 วินาที
- ขนาดแผ่นวงจรพิมพ์ : 2.12 x 3.59 นิว

การทำงานของวงจร

ในสภาวะปกติเมื่อยังไม่ยกหูโทรศัพท์ แรงไฟจากสายโทรศัพท์จะยังไม่สามารถผ่านโทรศัพท์เข้าสู่วงจรได้และเมื่อมีการยกหูโทรศัพท์ แรงไฟจะไหลผ่านโทรศัพท์ ผ่าน R1, D2 เข้ามา B ของ TR1 ทำให้ TR1 ทำงาน TR2 จึงทำงานส่งไฟไปเลี้ยงวงจร IC1 จึงเริ่มทำงานตัวเอง เมื่อถึงเวลาที่ตั้งไว้ท่า 3 ของ IC1 จะมีแรงไฟออกมายังหูฟัง R8 เข้า IC2/1 เพื่อสร้างเสียงเตือนและส่องไฟไป เข้า IC2/2,R10 และ TR4 เพื่อทำการขยายเสียง เตือนอีกรอบ แรงไฟที่ขา 3 ของ IC1 จะไหลผ่าน R7 ชาร์จขา C5 ประมาณ 3 ใน 4 ของไฟเดียว จะทำให้ท่า 10 ของ IC2/3 ที่จะเป็น LOW และลดลงไฟที่ขา 5 ของ IC2/1 จึงทำให้เสียงหยุดดัง C4 ก็จะหายใจรบกวนต่อค่าน R5 ให้เวลาประมาณ 20 วินาที ท่า 11 ของ IC2/4 จะมีแรงไฟออกมายังหูฟัง TR3 ทำให้ TR5 ที่จะทำงานด้วย TR1,TR2 จึงหยุดทำงาน แต่แรงไฟจะซึบลงเมื่อไฟแรงไฟฟ้าได้มาจาก TR5 แทน โทรศัพท์จะถูกตัดออกจากการโทรศัพท์และเมื่อไรวางหู โทรศัพท์ TR7 ก็จะหยุดทำงาน C10 ก็จะหายไปอีก 10 วินาที TR6 ก็จะหยุดทำงาน ทำให้ท่า 12 ของ IC1 ไฟไปรีเซ็ต IC1 ทำให้ท่า 3 ไม่ไฟที่ขา 10 ของ IC2/3 จึงเป็น HIGH และท่า 11 ของ IC2/4 ก็จะเป็น LOW ทำให้ TR3 และ TR5 หยุดทำงาน วงจรก็จะหยุดทำงานตามไปด้วย เพราะไม่มีแรงไฟไปเลี้ยงวงจร แค่มียกหูโทรศัพท์เมื่อใด วงจรก็จะเริ่มทำงานอีกรอบ

การประกอบวงจร

รูปการลงอุปกรณ์และการต่ออุปกรณ์ตามอย่างที่ระบุไว้ในรูปที่ 2 ในการประกอบวงจรควรเริ่มจากอุปกรณ์ที่มีความซับซ้อนอย่างมากก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยเริ่มจากไดโอดตามด้วยตัวแทนทานและไดโอดตามส่วนที่ต้องต่อลงบนวงจร ตามลำดับ เช่น ไนโตรดิโอด คากาซิสเตอร์แบบอิเล็กทรอนิกส์และทรานซิสเตอร์ เป็นต้น ควรใช้ความระมัดระวังในการประกอบวงจร ก่อนการใส่อุปกรณ์เหล่านี้จะต้องให้หัวที่ติดแผ่นวงจรพิมพ์กับหัวอุปกรณ์ให้ตรงกัน เพราะถ้าหากใส่กลับบ้านแล้ว อาจจะทำให้อุปกรณ์หรือวงจรเสียหายได้ วิธีการดูว่าและการใส่อุปกรณ์นั้นได้แมตต์ไฟไว้ในรูปที่ 3 แล้ว ในการบัดกรีให้หัวเรืองไฟไม่เกิน 40 วัตต์ และใช้ตัวบัดกรีที่มีอัตราเร็วของเทบูนและหัวที่ต้องร้อน ระหว่าง 60/40 รวมทั้งต้องเน้นยาประสานอย่างดีในตะกั่วด้วย หลังจากที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้ว ให้ทำการตรวจสอบความถูกต้องอีกครั้งหนึ่ง เพื่อให้เกิดความนิ่นใจแก่ตัวเรื่อง แต่หากติดต่ออุปกรณ์ติดตำแหน่ง ควรใช้ที่คุณต้องหันหรือล็อกขั้นตอนนี้ เพื่อป้องกันความเสียหายที่อาจจะเกิดกับสายวงจรพิมพ์ได้

การทดสอบ

ให้ต่อวงจรตามรูปที่ 2 แล้วปรับ VR1 มาทางซ้ายเมื่อสุด ให้ยกหูโทรศัพท์ LED1 จะติดและยกหูค้างไว้เป็นเวลาประมาณ 1 นาที จะได้เสียงเตือนประมาณ 2 วินาที และจะหยุดไปอีก 20 วินาที LED2 ก็จะติด ตอนนี้เสียงที่โทรศัพท์จะเริ่มไป และจะตัดสายโทรศัพท์ออกจากการโทรศัพท์และไว้หูประมาณ 10 วินาที LED1 และ LED2 จะดับ เมื่อยกหูโทรศัพท์อีกรอบ วงจรก็จะเริ่มทำงานใหม่อีกรอบ

การต่อใช้งาน

ให้ต่อตามรูป ที่จุด TEL IN จะต้องต่อสายจากเครื่องโทรศัพท์ ให้ถูกต้องด้วยสายหับการปรับเวลา สามารถปรับได้ตั้งแต่ 1 นาที จนถึงประมาณ 20 นาที โดยปรับที่กีดุม VR1

วงจรตีอัมและตัดสายโทรศัพท์ (ไม่ใช้ไฟ)

TELEPHONE CUT OFF TIMER 1-20 MIN.

CODE 322

LEVEL 2

Keeping control of your telephone bills or just reserving sufficient time for your calls when there are teenagers in the house, this circuit will give the phone hog a 2 seconds warning tone which if ignored will cut the line in 20 seconds. Access to the line is locked out for another 10 seconds.

Technical data

- No need power supply.
- Time range : from ± 1 to ± 20 minutes.
- There is a warning tone before cut off the tel line.
- Delay time before cut off : 20 seconds.
- IC board dimension : 2.12 in x 3.59 in.

How does it work

When the phone is off- hooked there will be a voltage at the base of TR1 (via R1, D2) and TR2 which then make the IC1 to start the countdown process. The warning signal also be generated when the predetermined duration (of the talking) is reached. In this case, the voltage from leg 3 of IC1 will enter leg 1 of IC2 (via R8) and finally to leg 2 of IC2, R10 and TR4 (for amplification work). The warning signal will eventually be stopped when the voltage at pin 3 of IC1 (via R7) charging C5 to 3/4 of its capacity (Vcc). This will drain the current at leg 10 and leg 5 of IC2 consecutively. Before the line is cut off, it will take C4 nearly 20 sec. to be fully charged (via R5). Pin 11 of IC2/4 will have enough voltage to make TR3 and TR5 active. TR1 and TR2 will not function even though the voltage at TR5 still remain.

When the phone is on- hooked, TR7 & TR6 will stop working while C10 took another 10 seconds to become fully discharged. The voltage at pin 12 of IC1 will resetting the IC1 so that there is no voltage at pin 3. This will make the voltage at pin 10 of IC2/3 high while the voltage at pin 11 of IC2/4 low (TR3 & TR5 also stop accordingly). Whenever the phone is picked up, the circuit will start working again.

Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolyte capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig. 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin- lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.

Testing

Install all component following figure 3. Adjust VR1 max. counter-clockwise. Picking the phone up, LED1 display, hold the line for 1 minute, there will be warning sound for 2 seconds and automatically stop, then LED2 will display after next 20 seconds, and the line will be cut off immediately. Hanging the phone for 10 seconds, LED1 and LED2 will stop. Whenever the phone is picked up, the circuit will start working again.

Application

Connected TEL IN as shown in figure 2. Time can be set for 1- 2 minutes by the trimmer potentiometer VR1.

Figure 1. The Telephone Cut Off Timer 1- 20 Min. Circuit


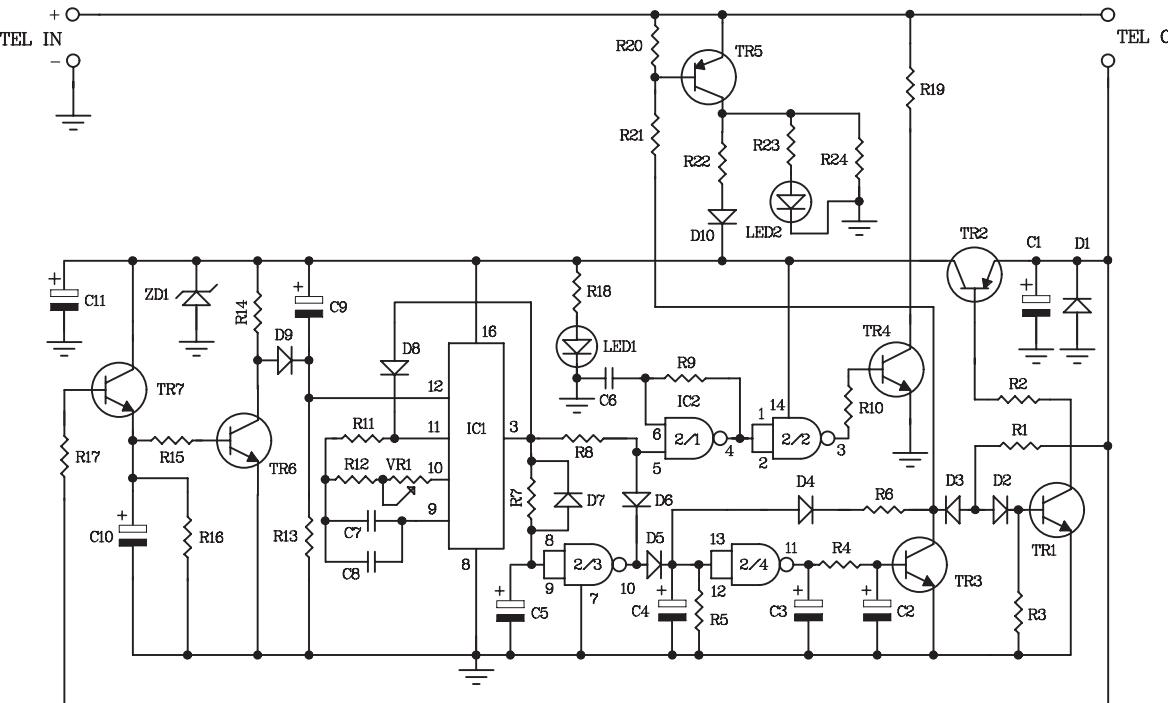


Figure 2. Circuit Assembling

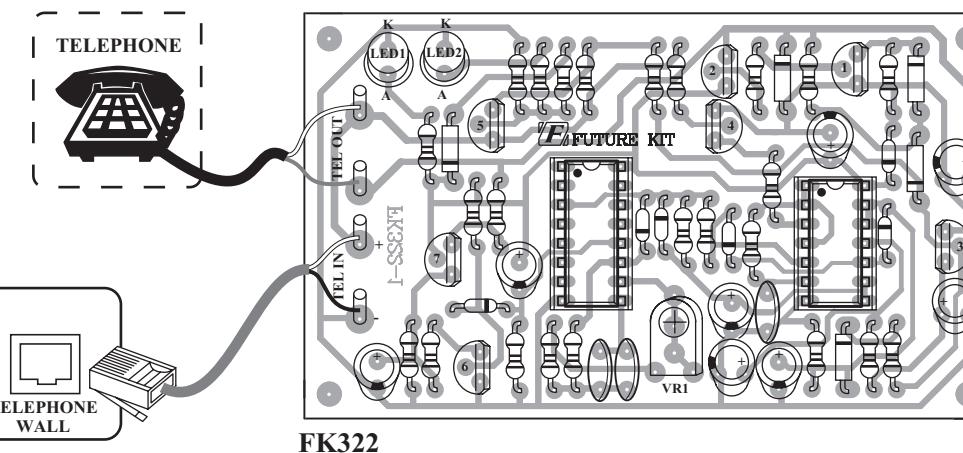

NOTE:

FUTURE BOX FB17
is suitable for this kit.

NO.1

Figure 3 . Installing the components

